

# CS2310: Final Assignment

## Computer System Design: Gajendra-I

Teammate1 :-

Name:- Prince Garg

Roll No. :- CS22B011


Teammate 2:-


Name:- Vikash Kumar Ojha

Roll No. :- CS22B013

### Section - 1 - ARCH\_GAJENDRA


Overall Architecture for CPU core:-

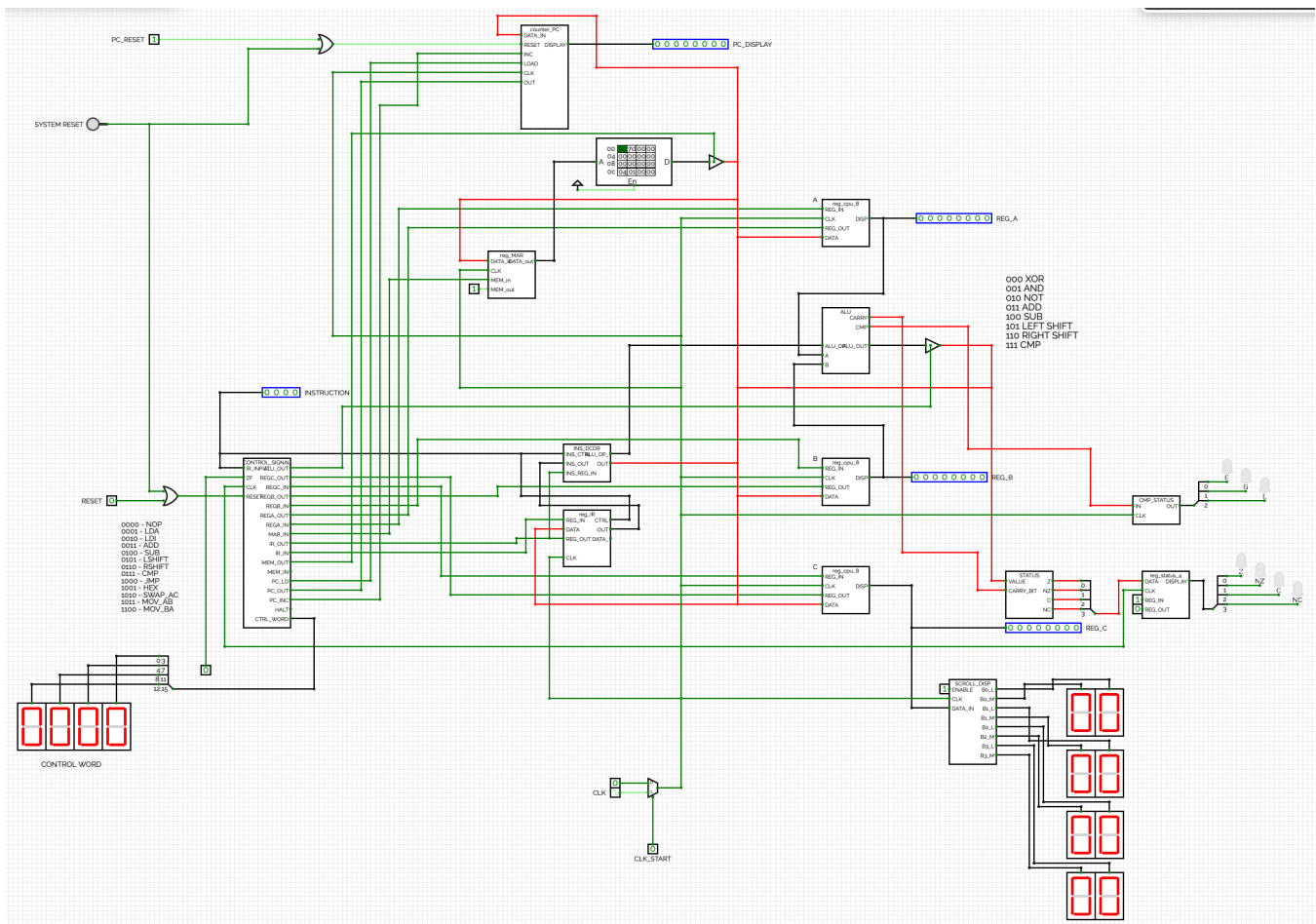

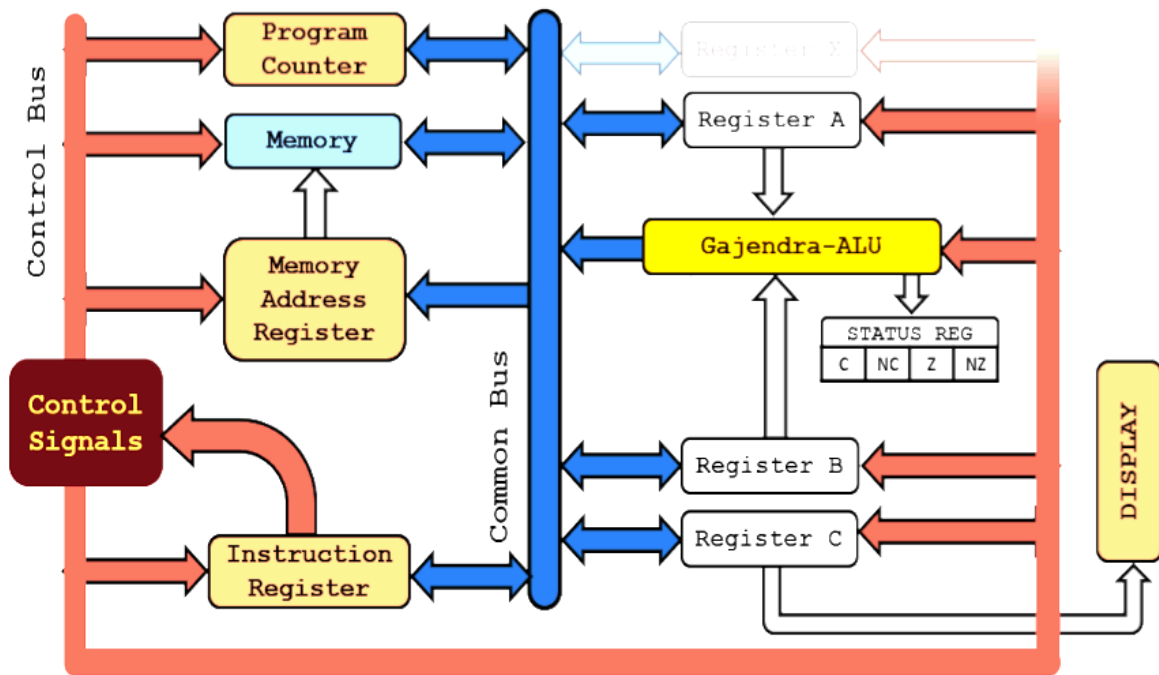


Various internal components used are:-

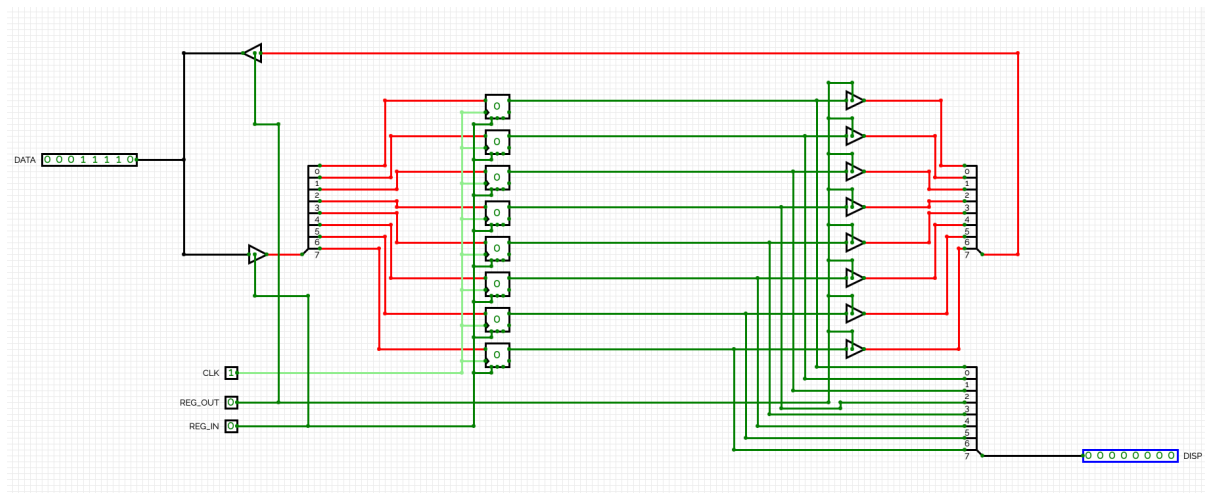
- 1) General CPU registers:- Stores 8-bit data for dynamic use.



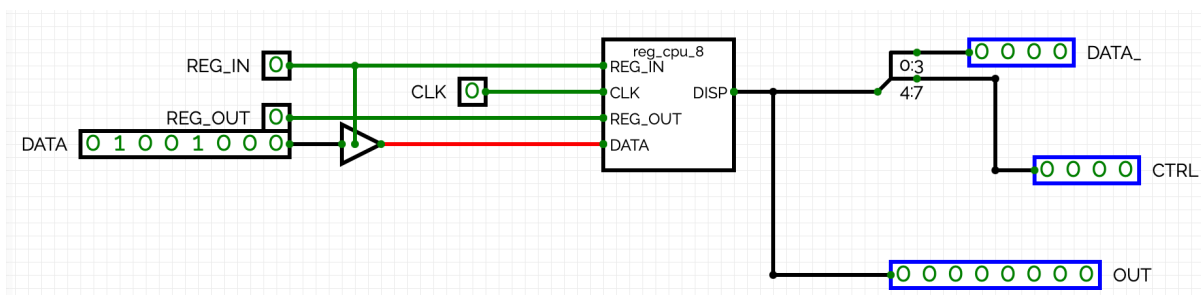
- 2) Instruction Register:- Separates instruction and data/address passed from the control word.



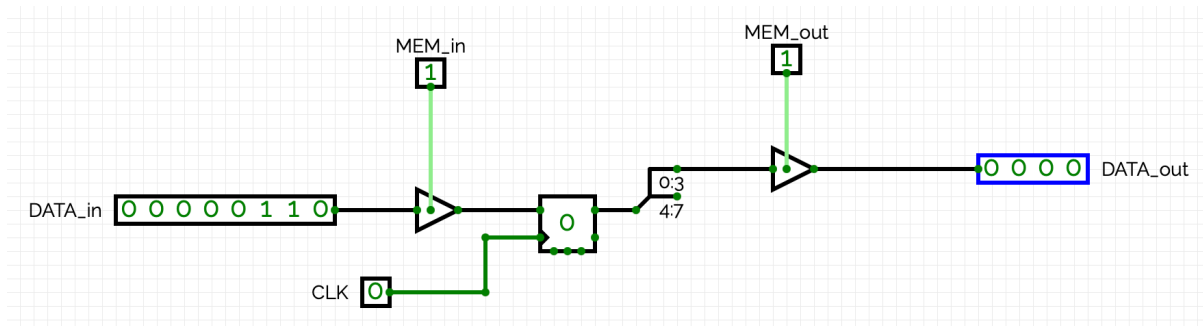3) Memory Address Register:- Stores the 4-bit address to be fetched from the ROM.



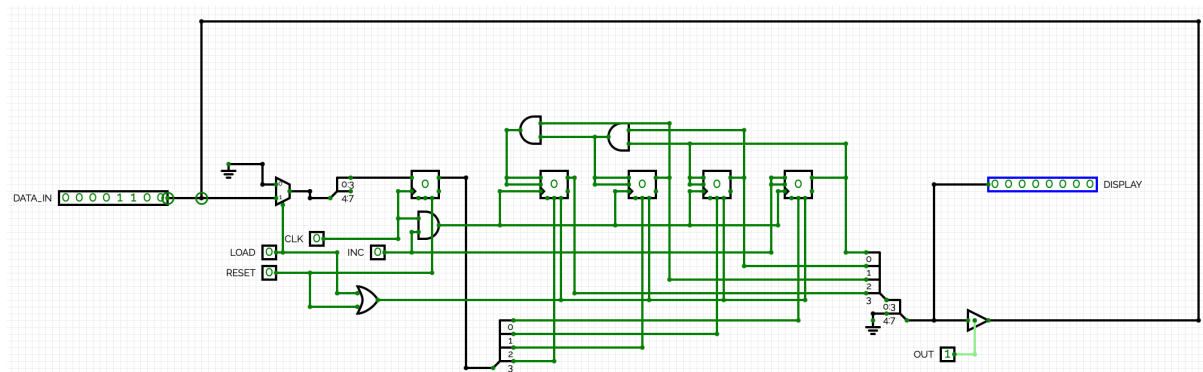4) Program Counter:- Stores, loads, increments and passes 4 bits indicating the opcode to be fetched from the ROM.




5) Arithmetic And Logical Unit:- Can perform various tasks for different ALU operation codes.

000	-	XOR
001	-	AND
010	-	NOT
011	-	ADD
100	-	SUB
101	-	LEFT SHIFT

110 - RIGHT SHIFT


111 - CMP

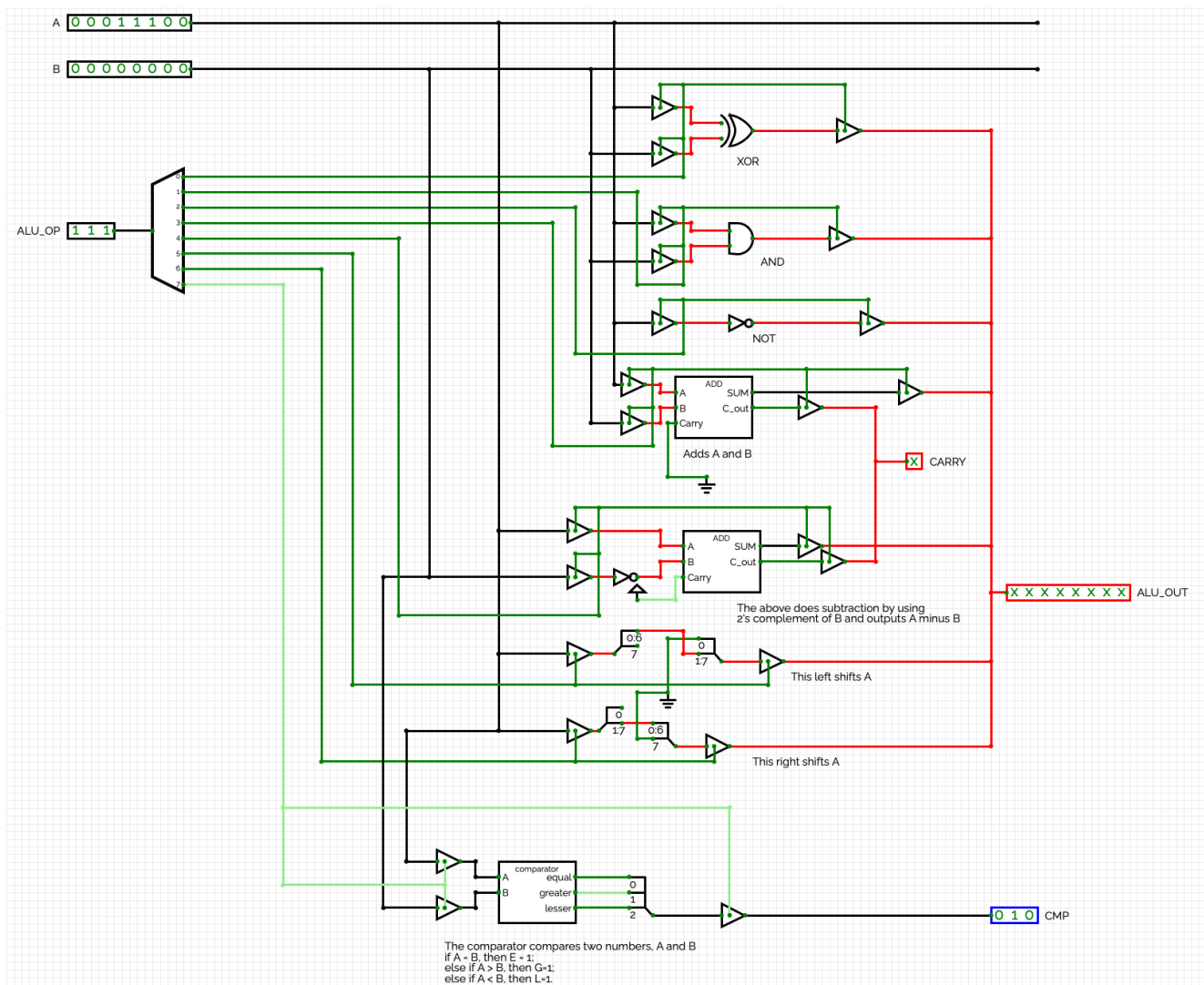

6) Status Register:- Gives the status of the output of operation done by ALU in true/false.

States if the bit is zero or nonzero and if the bit has a carry-over or not after MSB.

Status Register:-

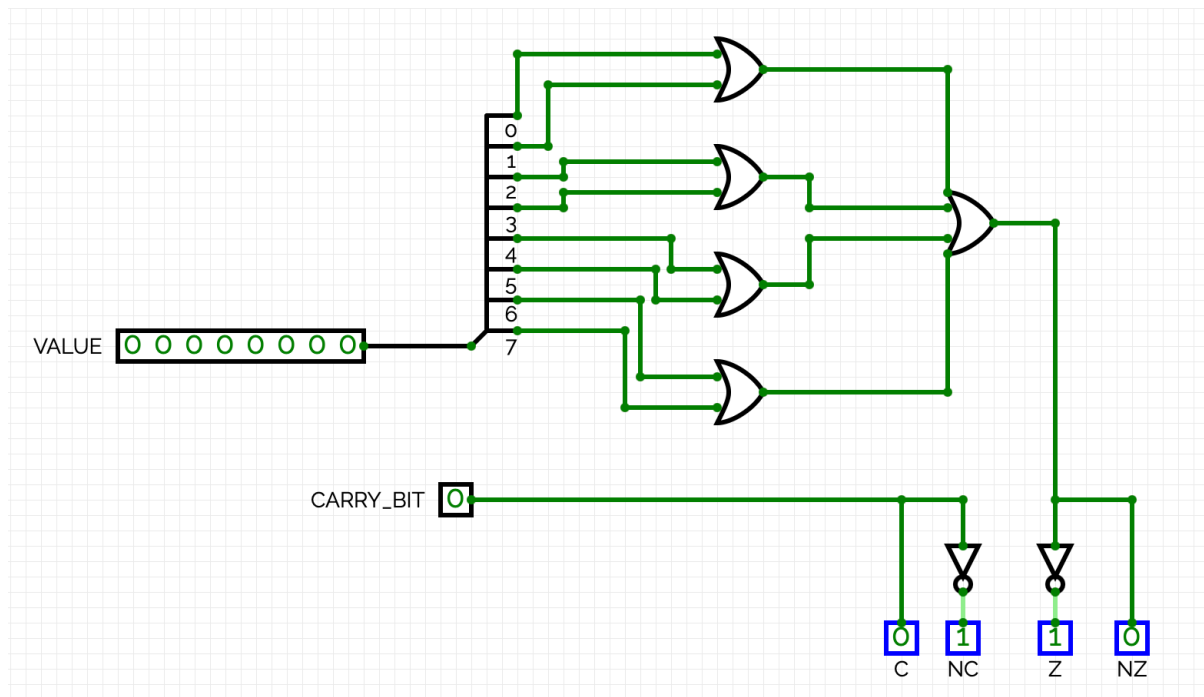

## Section - 2 - Defining Instruction Set

### 1) NOP - No Operation

#### Description:-

Performs single cycle no operation.

Operation:-

No operation

Syntax:-

NOP

Operands:-

None

Program Counter:-

$PC \leftarrow PC+1$

8-bit opcode:-

0000

0000

## **2) LDA - Load A(Accumulator)**

### **Description:-**

Loads the data from a given address into register A.

Operation:-

(i)  $A \leftarrow \text{MEM}[\text{Address}]$

Syntax:-

Operands:-

Program Counter:-

LDA Address

$0 \leq d \leq 15$

$PC \leftarrow PC+1$

8-bit opcode:-

0001

dddd

## **3) LDI - Load Immediate**

### **Description:-**

Loads specified data into register A.

Operation:-

(i)  $A \leftarrow \text{DATA}$

Syntax:-

Operands:-

Program Counter:-

LDI DATA

$0 \leq d \leq 15$

$PC \leftarrow PC+1$

8-bit opcode:-

0010

dddd

#### **4) ADD - Addition Without Carry**

##### **Description:-**

Adds value stored at the given address to register A without using the carry flag.

Operation:-

(i)  $B \leftarrow \text{MEM}[\text{Address}]$

(ii)  $A \leftarrow A + B$

Syntax:-

Operands:-

Program Counter:-

ADD Address

$0 \leq d \leq 15$

$PC \leftarrow PC + 1$

8-bit opcode:-

0011

dddd

#### **5) SUB - Subtraction Without Carry**

##### **Description:-**

Subtracts value stored at the given address from register A without using the carry flag.

Operation:-

(i)  $B \leftarrow \text{MEM}[\text{Address}]$

(ii)  $A \leftarrow A - B$

Syntax:-

Operands:-

Program Counter:-

SUB Address

$0 \leq d \leq 15$

$PC \leftarrow PC + 1$

8-bit opcode:-

0100

dddd

## 6) LSHIFT - LEFT SHIFT

### **Description:-**

Left shifts the value stored in register A(Accumulator) stores back to A.

Operation:-

$$(i) A \leftarrow (A \ll 1)$$

Syntax:-

Operands:-

Program Counter:-

LSHIFT

None

$PC \leftarrow PC+1$

8-bit opcode:-

0101

0000

## 7) RSHIFT - RIGHT SHIFT

### **Description:-**

Right shifts the value stored in register A(Accumulator) stores back to A.

Operation:-

$$(i) A \leftarrow (A \gg 1)$$

Syntax:-

Operands:-

Program Counter:-

RSHIFT

None

$PC \leftarrow PC+1$

8-bit opcode:-

0110

0000



## 8) **CMP - COMPARATOR**

### **Description:-**

Compares the value stored at the given address with the value stored in register A(Accumulator).

Sets flag:-

$L = 1$ ; if  $A < \text{MEM}[\text{Address}]$

$E = 1$ ; if  $A = \text{MEM}[\text{Address}]$

$G = 1$ ; if  $A > \text{MEM}[\text{Address}]$

Operation:-

(i)  $B \leftarrow \text{MEM}[\text{Address}]$

(ii) Compare and Set Flag

Syntax:-

Operands:-

Program Counter:-

CMP Address

$0 \leq d \leq 15$

$PC \leftarrow PC+1$

8-bit opcode:-

0111

dddd

## 9) **JMP - UNCONDITIONAL JUMP**

### **Description:-**

Changes the value of the program counter to the value specified.

Operation:-

(i)  $PC \leftarrow \text{ADDRESS}$

Syntax:-

Operands:-

Program Counter:-

JMP ADDRESS

$0 \leq d \leq 15$

$PC \leftarrow \text{ADDRESS}$

8-bit opcode:-

1000

dddd

## **10) HEX - DISPLAY OUTPUT**

### **Description:-**

Displays the value stored in register A as output via register C.

Operation:-

(i)  $C \leftarrow A$

Syntax:-

Operands:-

Program Counter:-

HEX

None

$PC \leftarrow PC+1$

8-bit opcode:-

1001

0000

## **11) SWAP\_AC -**

### **Description:-**

Swaps values of register A(Accumulator) and register C.

Operation:-

(i)  $B \leftarrow A$

(ii)  $A \leftarrow C$

(iii)  $C \leftarrow B$

Syntax:-

Operands:-

Program Counter:-

SWAP\_AC

None

$PC \leftarrow PC+1$

8-bit opcode:-

1010

0000

### **12) MOV\_AB - MOVE A to B**

#### **Description:-**

Moves value in register A(Accumulator) to register B.

Operation:-

(i)  $B \leftarrow A$

Syntax:-

Operands:-

Program Counter:-

MOV\_AB

None

$PC \leftarrow PC+1$

8-bit opcode:-

1011

0000

### **13) MOV\_BA - MOVE B to A**

#### **Description:-**

Moves value in register B to register A(Accumulator).

Operation:-

(i)  $A \leftarrow B$

Syntax:-

Operands:-

Program Counter:-

MOV\_BA

None

$PC \leftarrow PC+1$

8-bit opcode:-

1100

0000

**Instruction Set:-**

0000	-	NOP
0001	-	LDA
0010	-	LDI
0011	-	ADD
0100	-	SUB
0101	-	LSHIFT
0110	-	RSHIFT
0111	-	CMP
1000	-	JMP
1001	-	HEX
1010	-	SWAP_AC
1011	-	MOV_AB
1100	-	MOV_BA


***Section - 3 - Assembly Programs Examples***

1. Adding two numbers and displaying the result

Adding numbers stored at address 0xC and 0xD.  
Answer=0x05+0x07=0x0C=>00001100

Control Rom:-


Registers:-

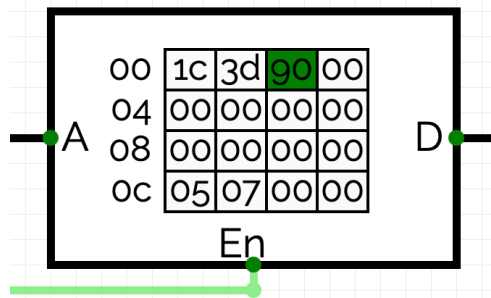

OUTPUT :- register C = 0x0C

PROGRAM:-
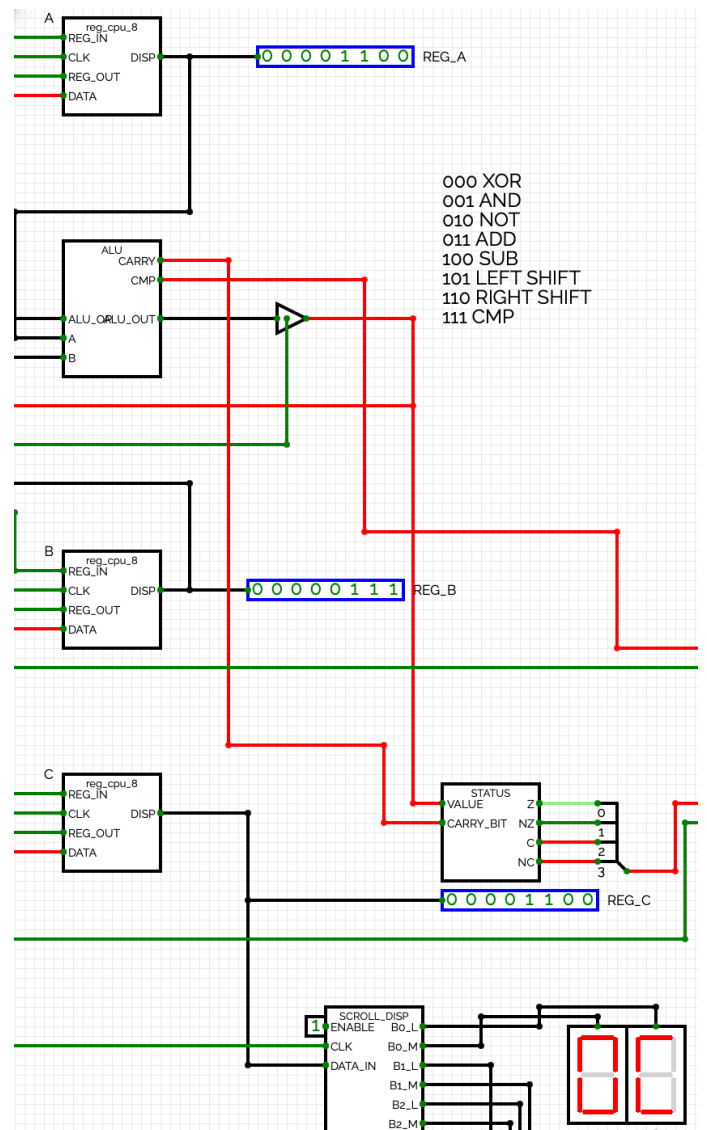
```
0x0  LDA  0xC
0x1  ADD  0xD
0x2  HEX
```



2. Adding and subtracting four numbers in some combination (e.g., 17-8+25-12)

Stored

17, i.e., 0x11 at 0xC


8, i.e., 0x08 at 0xD

25, i.e., 0x19 at 0xE

12, i.e., 0x0C at 0xF

Answer = 17-8+25-12 = 22 = 0x16

## Control ROM:-

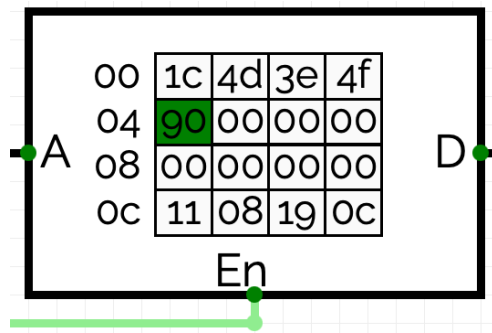


OUTPUT :- register C = 0x16

## PROGRAM:-

```


0x0  LDA  0xC
0x1  SUB  0xD
0x2  ADD  0xE
0x3  SUB  0xF
0x4  HEX
    
```

## Registers:-

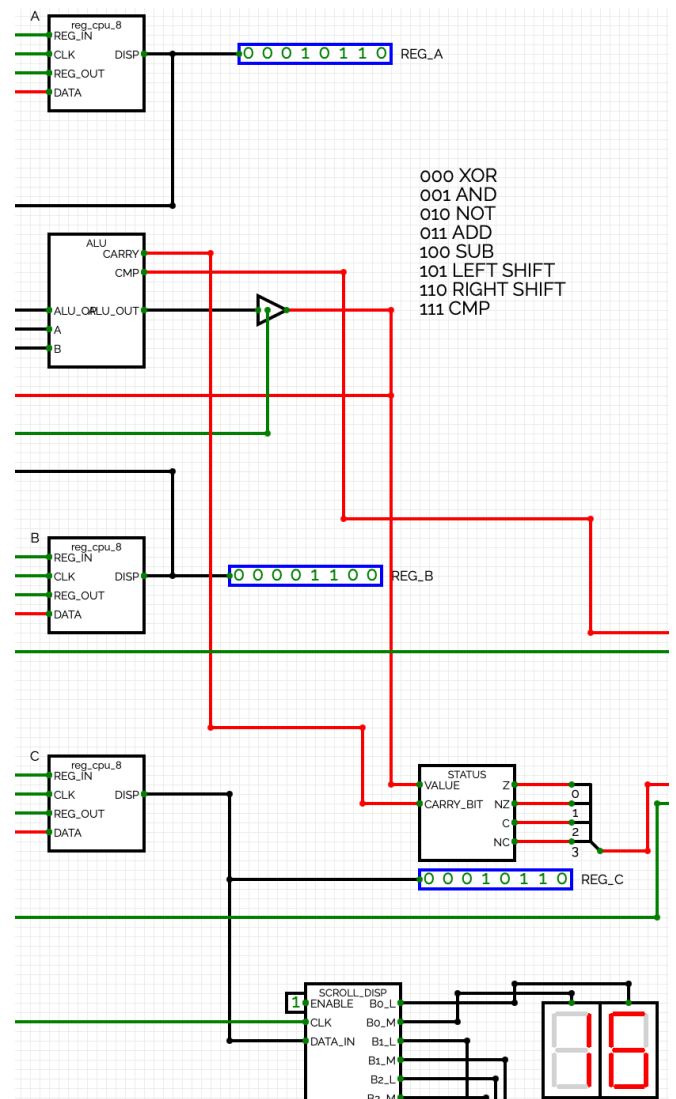


### 3. Display multiplication table for a number stored at some address.

Control ROM :-

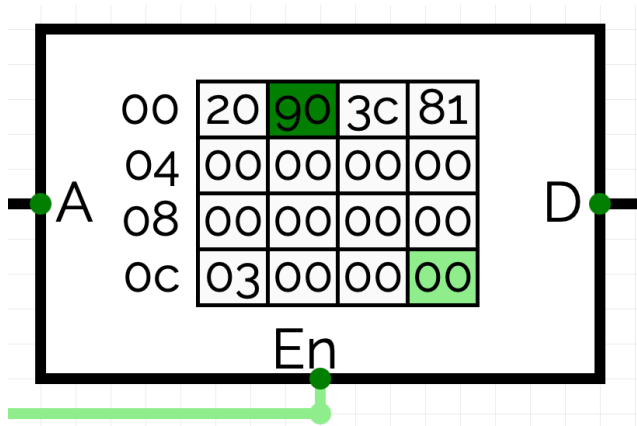

Registers:-

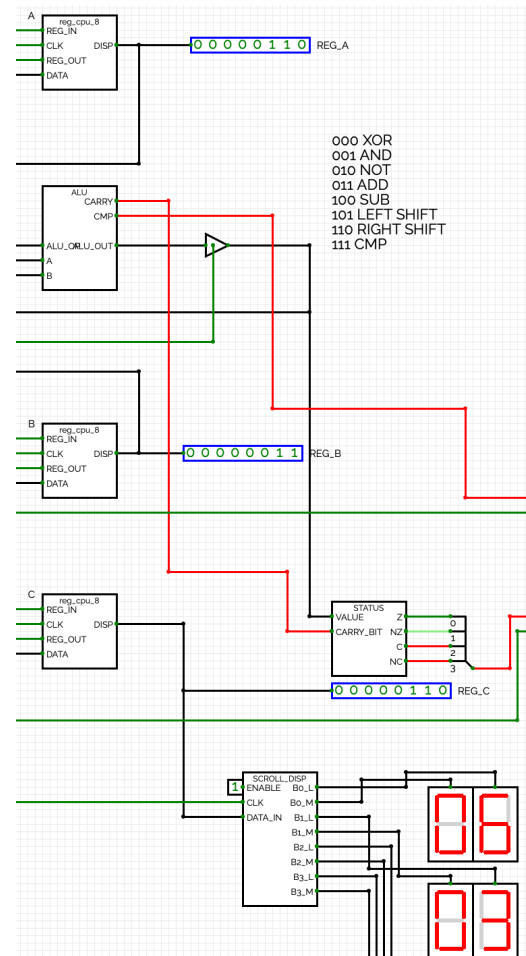

Output:- Register C:-

first it displays 0x00

next cycle :- 0x03

next :- 0x06

next :- 0x09

and so on...

PROGRAM:-

0x0 LDI 0x0

0x1 HEX

0x2 ADD 0xC

0x3 JMP 0x1

## Section - 4 - Microinstructions and controller logic design

	PC_INC	PC_OUT	PC_LOAD	MEM_IN	MEM_OUT	IR_IN	IR_OUT	MAR_IN	REGA_IN	REGA_OUT	REGB_IN	REGB_OUT	REGC_IN	REGC_OUT
T <sub>0</sub>	0	1	0	0	0	0	0	1	0	0	0	0	0	0
T <sub>1</sub>	1	0	0	0	1	1	0	0	0	0	0	0	0	0
T <sub>2</sub>														

Column Numbers:-

PC\_INC = 14

PC\_OUT = 13

PC\_LOAD = 12

MEM\_IN = 11

MEM\_OUT = 10

IR\_IN = 9

IR\_OUT = 8

MAR\_IN = 7

REGA\_IN = 6

REGA\_OUT = 5

REGB\_IN = 4


REGB\_OUT = 3

REGC\_IN = 2


REGC\_OUT = 1

ALU\_OUT = 0


NOP:- 0000

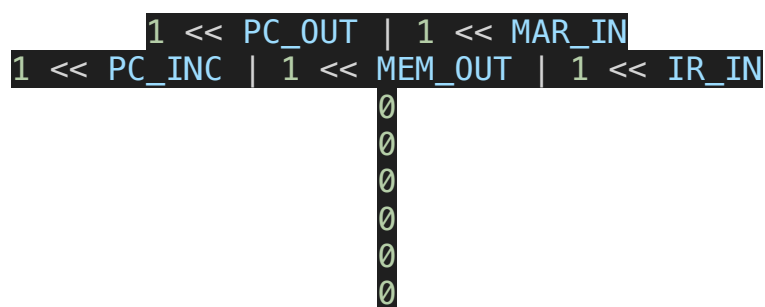


LDA:- 0001

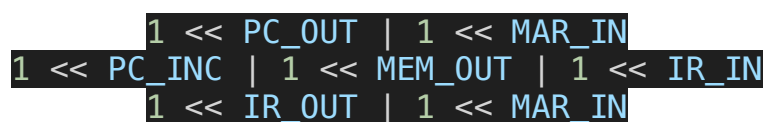




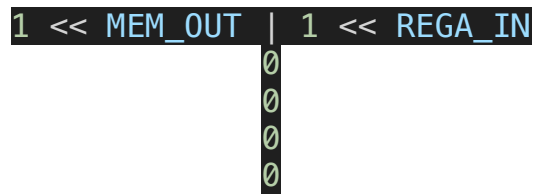


LDI:- 0010

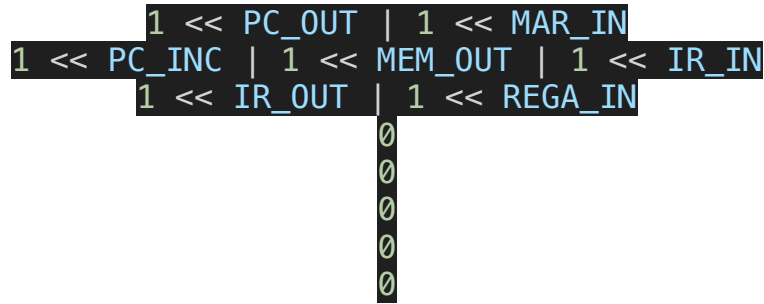


ADD:- 0011

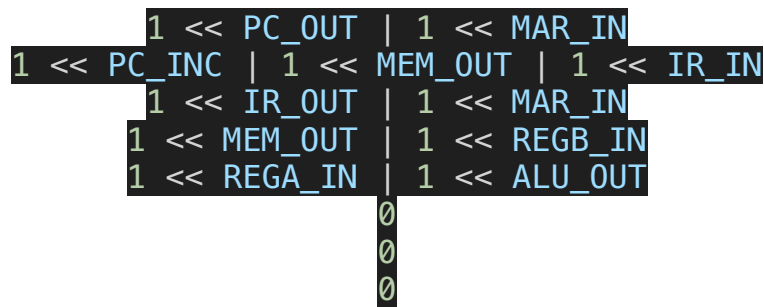

SUB:- 0100

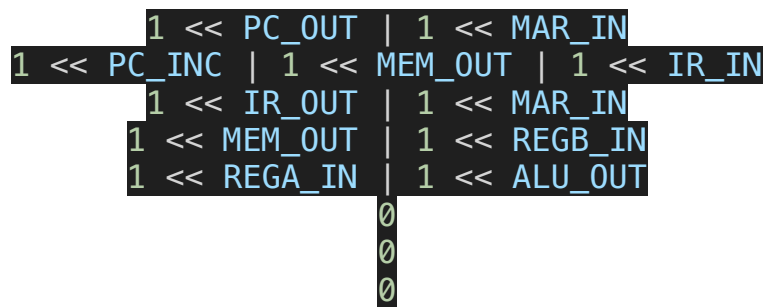

LSHIFT:- 0101

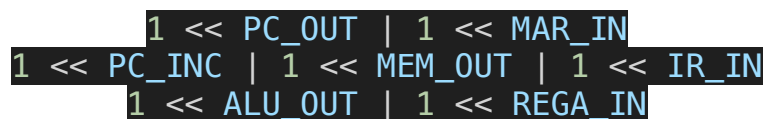

0  
0  
0  
0  
0

RSHIFT:- 0110

1 << PC_OUT		1 << MAR_IN
1 << PC_INC		1 << MEM_OUT   1 << IR_IN
1 << ALU_OUT		1 << REGA_IN

0  
0  
0  
0  
0

CMP:- 0111

1 << PC_OUT		1 << MAR_IN
1 << PC_INC		1 << MEM_OUT   1 << IR_IN
1 << IR_OUT		1 << MAR_IN
1 << MEM_OUT		1 << REGB_IN
1 << ALU_OUT		

0  
0  
0


JMP:- 1000

1 << PC_OUT		1 << MAR_IN
1 << PC_INC		1 << MEM_OUT   1 << IR_IN
1 << IR_OUT		1 << PC_LOAD


0  
0  
0  
0  
0

HEX:- 1001


1 << PC_OUT		1 << MAR_IN
-------------	--	-------------

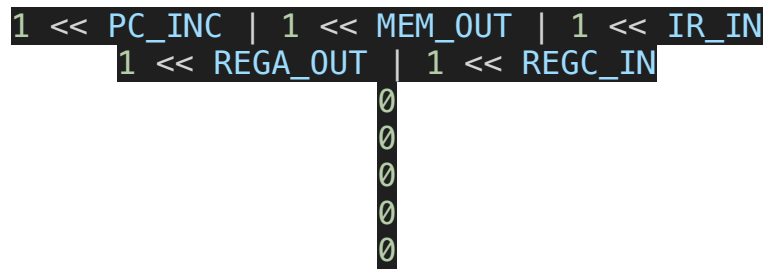


SWAP\_AC:- 1010

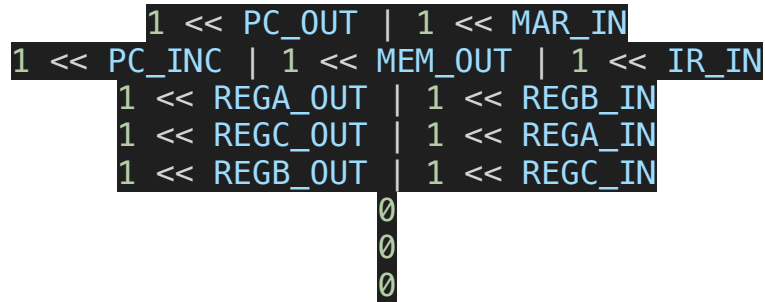

MOV\_AB:- 1011

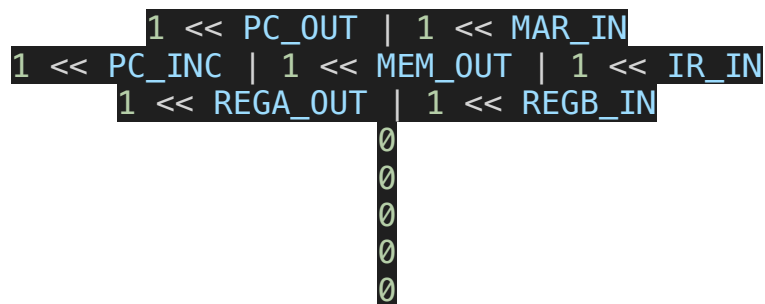


MOV\_BA:- 1100

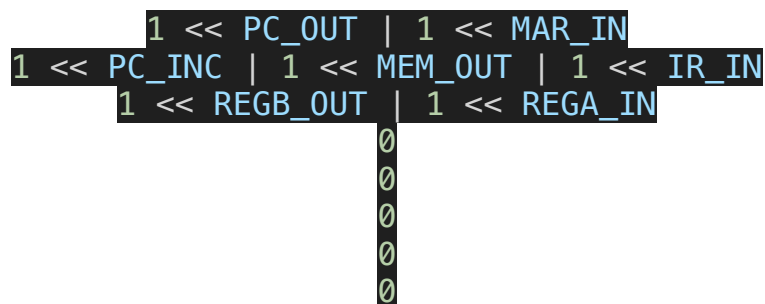

The minimum number of T-states needed for this instruction set is 5.  
However, we have used 8 T-states for each instruction.
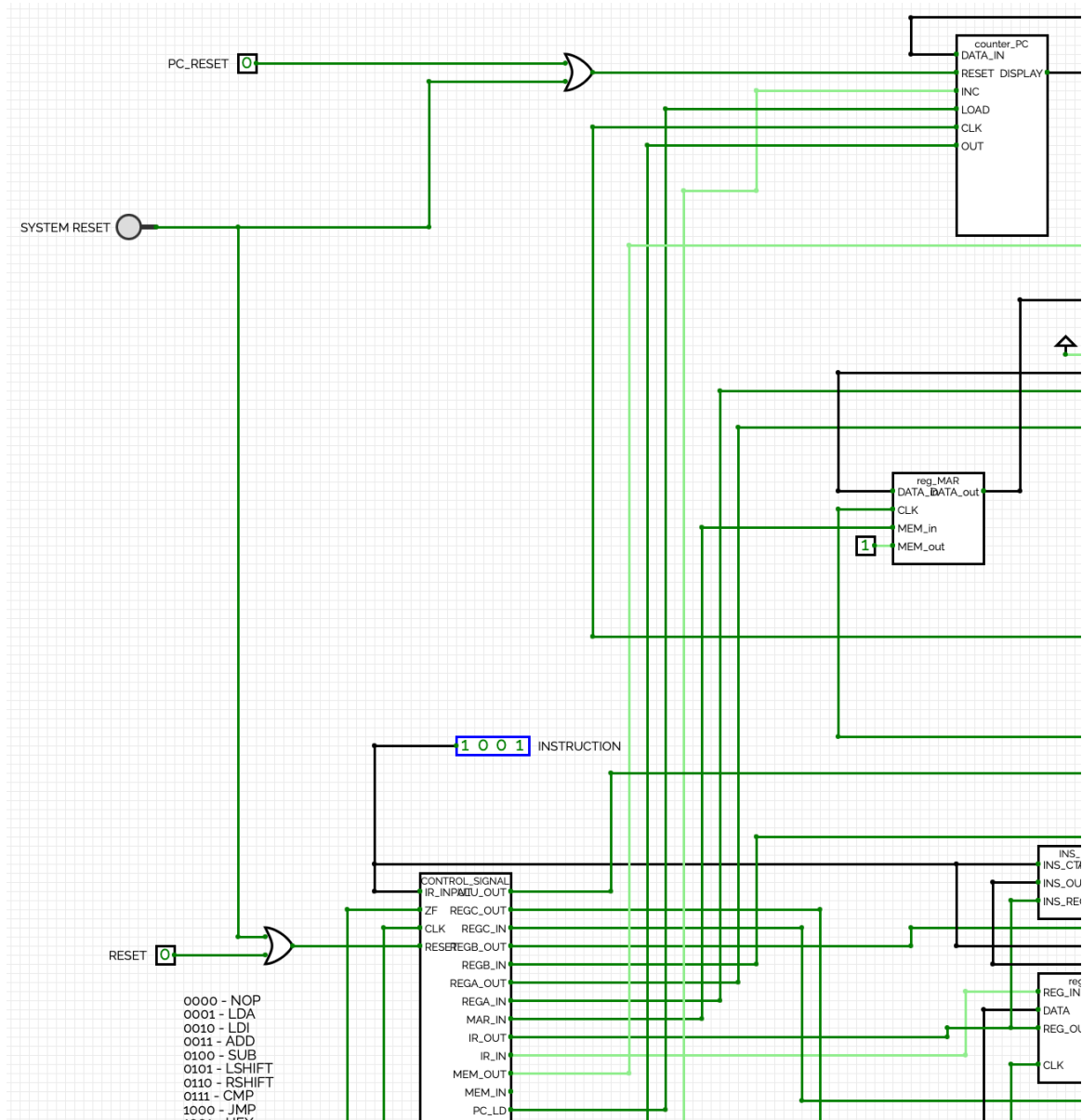
## Section - 5 - System Reset

**System Reset:-** Reset button that reboots the computer to execute instructions from address 0x0. It also resets the PC count to zero and the controller's internal counter.



## Additional (extra credits) Extension


1)[Simple] Update the ALU to support instructions like CMP (compare), SWAP, some MOV instructions, SHIFT (Left/Right) etc. A program must be written to demonstrate the capability of such instructions.

—> Updated the ALU to support CMP, SWAP\_AC, MOV\_AB, MOV\_BA, LSHIFT and RSHIFT functions also.


—> Wrote C program for the instruction set and updated the EEPROM to contain the instructions.

Ques:- Fetch two numbers stored in memory, left shift one, compare them and print one by one.

Control ROM :-

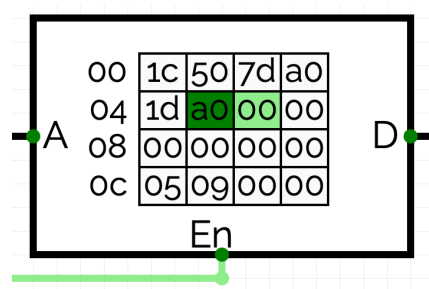

Registers:-

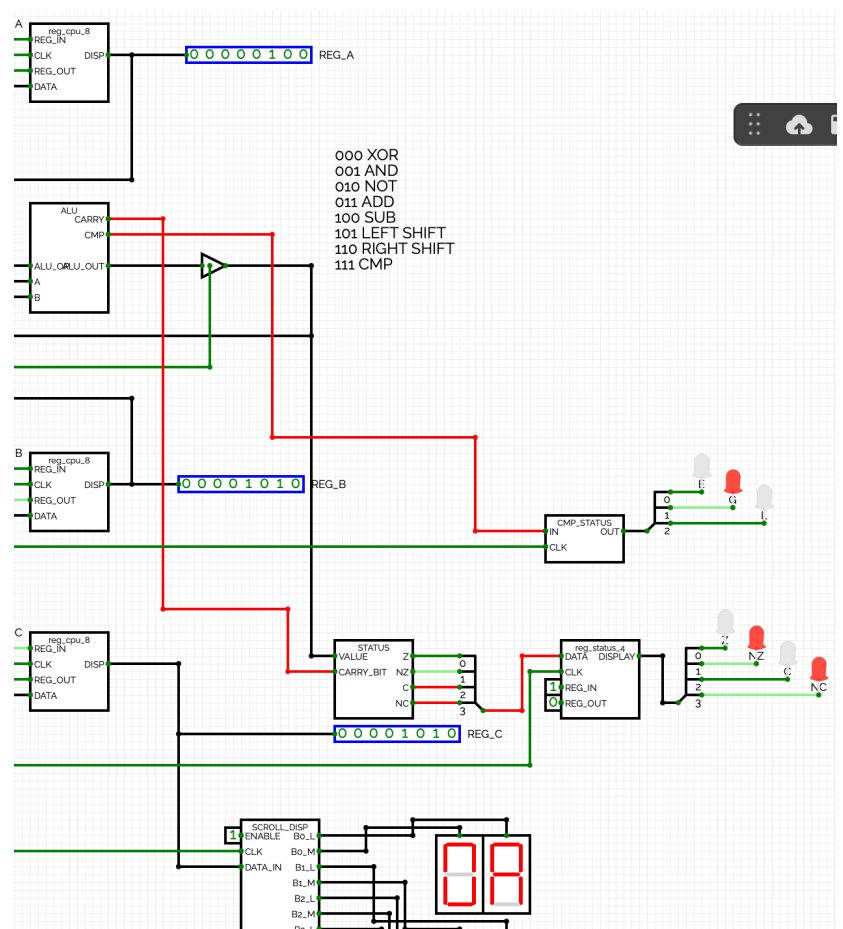

OUTPUT:-

left shift of 0x05 = 0x0A

0x0A > 0x09 hence, G flag is set to 1.

PROGRAM:-

```

0x0  LDA      0xC
0x1  LSHIFT
0x2  CMP      0xD
0x3  SWAP_AC
0x4  LDA      0xD
0x5  SWAP_AC
  
```

